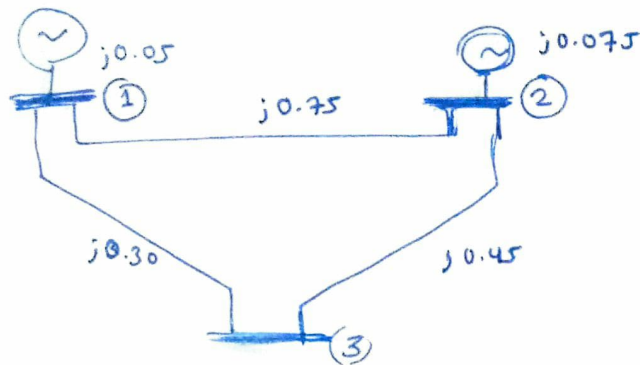


1.



- $Z_{bus} = []$
- Add new bus (1) to ref. via $z = j0.05$ (I)

$$Z_{bus} = j[0.05]$$

- Add new bus (2) to ref. via $z = j0.075$ (I)

$$Z_{bus} = j \begin{bmatrix} 0.0500 & 0.0000 \\ 0.0000 & 0.0750 \end{bmatrix}$$

- Add link b/w of $z = j0.75$ b/w existing buses (1) and (2) (IV)

$$\Delta Z = [Z_{bus}(:,1) - Z_{bus}(:,2)] = j \begin{bmatrix} 0.0500 \\ -0.0750 \end{bmatrix}$$

$$Z_{LL} = Z_{bus}(1,1) + Z_{bus}(2,2) - 2Z_{bus}(1,2) + z$$

$$\text{or } Z_{LL} = j0.8750$$

$$Z_{bus}^{new} = Z_{bus} - \frac{\Delta Z \Delta Z^T}{Z_{LL}}$$

1/7

$$\text{or } Z_{bus}^{new} = j \begin{bmatrix} 0.0470 & 0.0043 \\ 0.0043 & 0.0686 \end{bmatrix}$$

- Add new bus ③ to existing bus ① via $z = j0.30$ (II)

$$Z_{bus} = j \begin{bmatrix} 0.0471 & 0.0043 & 0.0471 \\ 0.0043 & 0.0686 & 0.0043 \\ 0.0471 & 0.0043 & 0.3471 \end{bmatrix}$$

- Add a link of $z = j0.45$ b/w existing buses ② and ③ (IV):

$$Z_{bus} = j \begin{bmatrix} 0.0450 & 0.0075 & 0.0300 \\ 0.0075 & 0.0638 & 0.0300 \\ 0.0300 & 0.0300 & 0.2100 \end{bmatrix}$$

Symmetrical fault at bus ③, $Z_f = j0.19$!

* For unloaded generators, $V_0 = \begin{bmatrix} 1.00 \\ 1.00 \\ 1.00 \end{bmatrix}$ (pre-fault voltage).

Fault current (at bus ③): $I_{3f} = \frac{V_0(3)}{Z_{bus(3,3)} + Z_f}$

$$\text{or } \boxed{I_{3f} = -j2.5000} \text{ Am}$$

During
Post fault voltages:

$$V = V_0 - \frac{Z_{bus}(2,3)}{Z_{bus}(3,3) + Z_f} \cdot V_0$$

or

$$V = \begin{bmatrix} 0.9250 \\ 0.9250 \\ 0.4750 \end{bmatrix} \text{ Ans}$$

Line current during fault:

$$I_{12} = \frac{V(1) - V(2)}{Z_{12}} = 0$$

$$I_{13} = \frac{V(1) - V(3)}{Z_{13}} = -j1.5000$$

$$I_{23} = \frac{V(2) - V(3)}{Z_{23}} = -j1.0000$$

Ans

—————X—————X—————

2.

$$I_a^{012} = \begin{bmatrix} 3 \angle -30^\circ \\ 5 \angle 90^\circ \\ 4 \angle 30^\circ \end{bmatrix}$$

$$I^{abc} = A I_a^{012} = \begin{bmatrix} 8.1854 \angle 42.2163^\circ \\ 4.0000 \angle -30.0000^\circ \\ 8.1854 \angle -102.2163^\circ \end{bmatrix}$$

Ans.

$$\text{where } A = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix}$$

$$\alpha = 1 \angle 120^\circ$$

3. Converting balanced Y load to balanced Δ load and drawing the circuit. (Fig. 2)

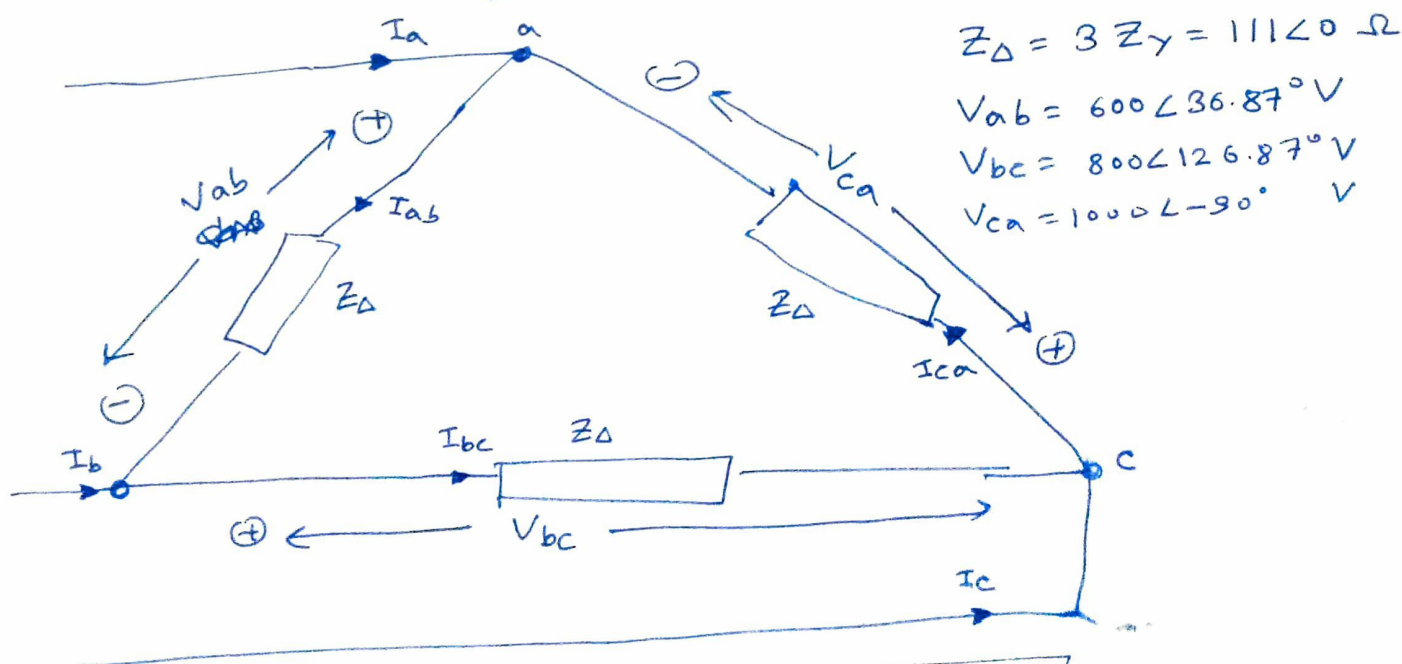


Fig. 2: Delta configuration

(a) < will be shown later >

(b) < will be shown later >

(c) Line currents:

$$\begin{aligned} \text{(c)} \quad I_a &= I_{ab} - I_{ca} = \frac{V_{ab} - V_{ca}}{Z_{\Delta}} = 12.9930 \angle 70.5600^\circ \text{ A} \\ I_b &= I_{bc} - I_{ab} = \frac{V_{bc} - V_{ab}}{Z_{\Delta}} = 9.0090 \angle 163.7333^\circ \text{ A} \\ I_c &= I_{ca} - I_{bc} = \frac{V_{ca} - V_{bc}}{Z_{\Delta}} = 15.3946 \angle -73.6861^\circ \text{ A} \end{aligned}$$

Ans

Converting ckt. back to original Y connected load.

(b)

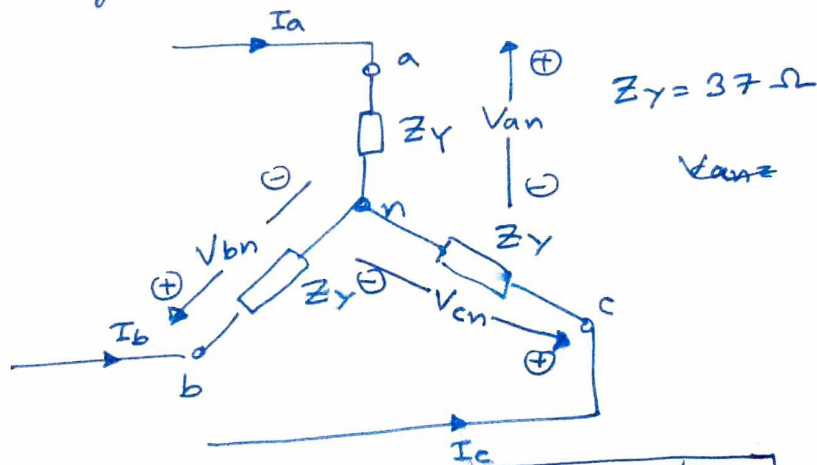


Fig. 2: Star configuration

(b) Phase voltages:

$$\text{(b)} \quad V^{abc} = \begin{bmatrix} V_{an} \\ V_{bn} \\ V_{cn} \end{bmatrix} = \begin{bmatrix} I_a Z_Y \\ I_b Z_Y \\ I_c Z_Y \end{bmatrix} = \begin{bmatrix} 480.7404 \angle 70.5600^\circ \text{ V} \\ 333.3333 \angle 163.7333^\circ \text{ V} \\ 569.6001 \angle -73.6861^\circ \text{ V} \end{bmatrix}$$

Ans

(a) The symmetrical components of voltage.

As it isn't clear which voltage (phase or line) and which phase (a/b/c or ab/bc/ca) is required, all components are derived here.

Sequence phase voltages are:

$$V_a^{012} = A^{-1} V^{abc} = \begin{bmatrix} 0.0000 \angle 180.0000^\circ \text{ V} \\ 136.8760 \angle 139.9342^\circ \text{ V} \\ 451.0955 \angle 54.0621^\circ \text{ V} \end{bmatrix}$$

where

$$A^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix}$$

$$\alpha = 1 \angle 120^\circ$$

$$V_b^{012} = \begin{bmatrix} V_a^0 \\ V_a^1 \angle -120^\circ \\ V_a^2 \angle 120^\circ \end{bmatrix} = \begin{bmatrix} 0.0000 \angle 180.0000^\circ \text{ V} \\ 136.8760 \angle 19.9342^\circ \text{ V} \\ 451.0955 \angle 174.0621^\circ \text{ V} \end{bmatrix}$$

$$V_c^{012} = \begin{bmatrix} V_a^0 \\ V_a^1 \angle 120^\circ \\ V_a^2 \angle -120^\circ \end{bmatrix} = \begin{bmatrix} 0.0000 \angle 180.0000^\circ \text{ V} \\ 136.8760 \angle 259.9342^\circ \text{ V} \\ 451.0955 \angle -65.9378^\circ \text{ V} \end{bmatrix}$$

Ans ly, ~~line~~ sequence line voltages are:

$$V_{ab}^{012} = A^{-1} \begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} = \begin{bmatrix} 0.0000 \angle 0.0000^\circ \text{ V} \\ 237.0762 \angle 169.9342^\circ \text{ V} \\ 781.3204 \angle 24.0621^\circ \text{ V} \end{bmatrix}$$

$$V_{bc}^{012} = \begin{bmatrix} 0.0000 \angle 0.0000^\circ \text{ V} \\ 237.0762 \angle 49.9342^\circ \text{ V} \\ 781.3204 \angle 144.0621^\circ \text{ V} \end{bmatrix}$$

$$V_{ca}^{012} = \begin{bmatrix} 0.0000 \angle 0.0000^\circ \text{ V} \\ 237.0762 \angle -70.0658^\circ \text{ V} \\ 781.3204 \angle -95.9379^\circ \text{ V} \end{bmatrix}$$

Ans

— X — X —
END OF ASSIGNMENT